

In the first example of a second-order circuit we worked out in class, we came up with the following differential equation for  $i(t)$ :

$$\frac{d^2i}{dt^2} + 6\frac{di}{dt} + 25i = 0$$

Using a trial solution of  $i(t) = Ae^{\lambda t}$ , the following characteristic equation is obtained:

$$\lambda^2 + 6\lambda + 25 = 0$$

Using the quadratic equation, we have the following solution:

$$\lambda = -3 \pm 4i$$

So, taking both solutions into account,  $i(t)$  becomes:

$$i(t) = Ae^{-3t + 4it} + Be^{-3t - 4it}$$

Factoring out the common  $e^{-3t}$  term and using Euler's identity, we end up with:

$$i(t) = e^{-3t} (Ae^{4it} + Be^{-4it}) = e^{-3t} (A \cos 4t + iA \sin 4t + B \cos 4t - iB \sin 4t) \quad (1)$$

Applying the initial condition of  $i(0) = 0$ , we get the following equation:

$$i(0) = e^0 (A \cos 0 + iA \sin 0 + B \cos 0 - iB \sin 0) = A + B = 0$$

So  $A = -B$ . Applying this result to equation (1) gives us:

$$i(t) = e^{-3t} (A \cos 4t + iA \sin 4t - A \cos 4t + iA \sin 4t) = e^{-3t} (2A i \sin 4t)$$

The goal, remember, was to find the voltage across the capacitor. Since  $i(t) = C \frac{dv}{dt}$ , we can find an expression for  $v(t)$ :

$$v(t) = \frac{1}{C} \int i(t) dt = \frac{1}{0.04} \int 2Aie^{-3t} \sin(4t) dt = 50Ai \int e^{-3t} \sin(4t) dt$$

To find the integral, we integrate by parts (recall:  $\int u dv = uv - \int v du$ )

$$\int e^{-3t} \sin(4t) dt = e^{-3t} \frac{-1}{4} \cos 4t - \int \frac{3}{4} e^{-3t} \cos(4t) dt$$

$$(\text{let } u = e^{-3t} \text{ and } dv = \sin 4t dt \dots \text{then } du = -3e^{-3t} dt \text{ and } v = -(\cos 4t) / 4)$$

Integrating by parts one more time (for the integral on the right hand side) gives us:

$$\int e^{-3t} \sin(4t) dt = -\frac{1}{4} e^{-3t} \cos 4t - \frac{3}{4} \int e^{-3t} \cos(4t) dt$$

$$\int e^{-3t} \sin(4t) dt = -\frac{1}{4} e^{-3t} \cos 4t - \frac{3}{4} \left[ \frac{1}{4} e^{-3t} \sin 4t + \int \frac{3}{4} e^{-3t} \sin(4t) dt \right]$$

(let  $u = e^{-3t}$  and  $dv = \cos 4t dt$ ...then  $du = -3e^{-3t} dt$  and  $v = (\sin 4t) / 4$ )

We can rearrange the equation and “solve” for the integral:

$$\int e^{-3t} \sin(4t) dt = -\frac{1}{4} e^{-3t} \cos 4t - \frac{3}{16} e^{-3t} \sin 4t - \frac{9}{16} \int e^{-3t} \sin(4t) dt$$

$$\frac{25}{16} \int e^{-3t} \sin(4t) dt = -\frac{1}{4} e^{-3t} \cos 4t - \frac{3}{16} e^{-3t} \sin 4t$$

$$\int e^{-3t} \sin(4t) dt = -\frac{4}{25} e^{-3t} \cos 4t - \frac{3}{25} e^{-3t} \sin 4t + K$$

where  $K$  is the integration constant (alternatively, you could look up this integral in a table)

So  $v(t)$  can be written now as:

$$v(t) = 50Ai \left[ -\frac{4}{25} e^{-3t} \cos 4t - \frac{3}{25} e^{-3t} \sin 4t + K \right]$$

$$v(t) = -2Aie^{-3t} [4 \cos 4t + 3 \sin 4t] + 50AiK$$

To find  $K$ , use the steady state value, i.e.  $v(\infty) = 12$

$$v(t) = 12 = -2Aie^{-\infty} [4 \cos \infty + 3 \sin \infty] + 50AiK = -2Ai[4 \cos \infty + 3 \sin \infty] + 50AiK$$

$$12 = 0 + 50AiK = 50AiK$$

So  $v(t) = -2Aie^{-3t} [4 \cos 4t + 3 \sin 4t] + 12$

To find  $A$ , use the other initial condition, i.e.  $v(0) = 0$

$$v(0) = 0 = -2Aie^0 [4 \cos 0 + 3 \sin 0] + 12 = -2Ai[4 + 0] + 12 = -8Ai + 12$$

$$0 = -8Ai + 12$$

$$8Ai = 12$$

$$A = \frac{12}{8i} = \frac{3}{2i}$$

So  $v(t) = -2\frac{3}{2i}ie^{-3t}[4\cos 4t + 3\sin 4t] + 12$   
 $v(t) = -3e^{-3t}[4\cos 4t + 3\sin 4t] + 12$   
 $v(t) = 12 - e^{-3t}[12\cos 4t + 9\sin 4t]$

This is exactly the same result we got in class after re-solving the problem (by converting  $i(t)$  in the KCL equation to  $v(t)$  using the IV relationship for the capacitor). Obviously, this approach takes more time and effort, but you get the same result, as expected.